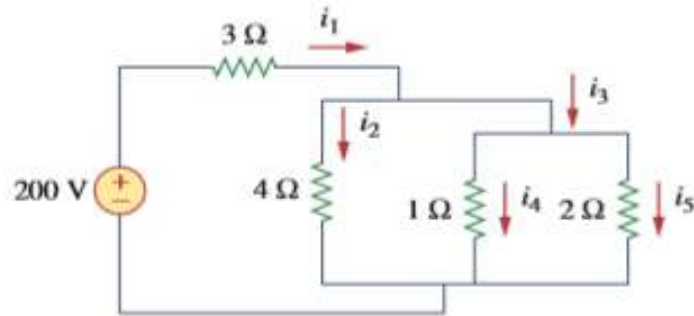


DC CIRCUIT

1. Find out the value of I_5, I_4, I_3, I_2, I_1 ?



Solution: Total resistance $R_T = (2 \parallel 1) + 4 = 3.571\Omega$

$$I_1 = \frac{200}{3.571} = 56A \quad (\text{Ans.})$$

$$V_4 = 200 - (56 \times 3) = 32V$$


$$I_2 = \frac{32}{4} = 8A \quad (\text{Ans.})$$

$$I_3 = 56 - 8 = 48A \quad (\text{Ans.})$$

$$I_4 = \frac{48 \times 2}{2+1} = 32A \quad (\text{Ans.})$$

$$I_5 = 48 - 32 = 16A \quad (\text{Ans.})$$

2. Find out the value of R .

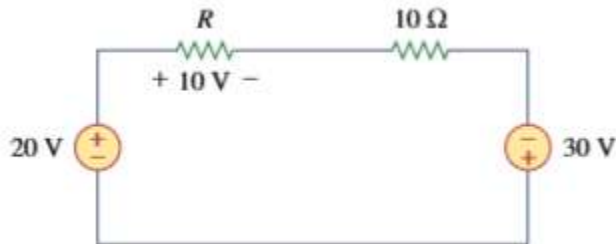

Solution: Apply KVL,


$$-20 + 10 + 10I - 30 = 0$$

$$I = 4A$$

$$R = \frac{10}{4} = 2.5\Omega \quad (\text{Ans.})$$

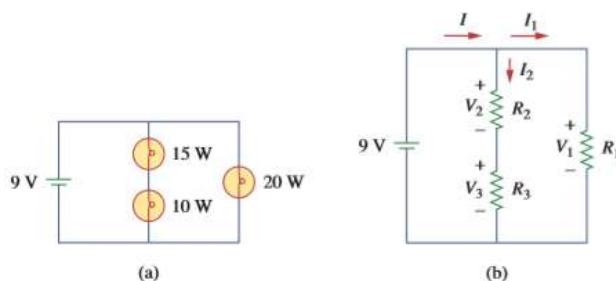3. Find out the value

Three light bulbs are connected to a 9-V battery as shown in Fig. 2.56(a). Calculate: (a) the total current supplied by the battery, (b) the current through each bulb, (c) the resistance of each bulb.



Solution:

(a) The total power supplied by the battery is equal to the total power absorbed by the bulbs; that is,

$$p = 15 + 10 + 20 = 45 \text{ W}$$

Since $p = VI$, then the total current supplied by the battery is

$$I = \frac{p}{V} = \frac{45}{9} = 5 \text{ A}$$

(b) The bulbs can be modeled as resistors as shown in Fig. 2.56(b). Since R_1 (20-W bulb) is in parallel with the battery as well as the series combination of R_2 and R_3 ,

$$V_1 = V_2 + V_3 = 9 \text{ V}$$

The current through R_1 is

$$I_1 = \frac{p_1}{V_1} = \frac{20}{9} = 2.222 \text{ A}$$

By KCL, the current through the series combination of R_2 and R_3 is

$$I_2 = I - I_1 = 5 - 2.222 = 2.778 \text{ A}$$


(c) Since $p = I^2 R$,

$$R_1 = \frac{p_1}{I_1^2} = \frac{20}{2.222^2} = 4.05 \Omega$$

$$R_2 = \frac{p_2}{I_2^2} = \frac{15}{2.777^2} = 1.945 \Omega$$


$$R_3 = \frac{p_3}{I_3^2} = \frac{10}{2.777^2} = 1.297 \Omega$$

4. Find out the value of R

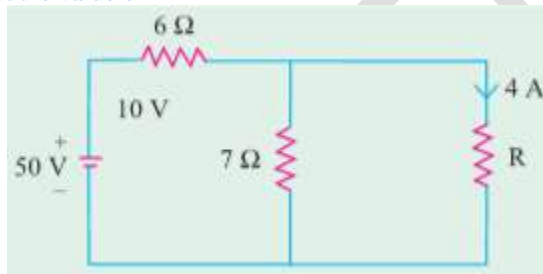

Solution: $V_R = 50 - 10 = 40\text{V}$
 $R = \frac{40}{4} = 10\Omega$ Ans.

5. Find out the value of V & $P_{1\Omega}$ apply super position theorem.

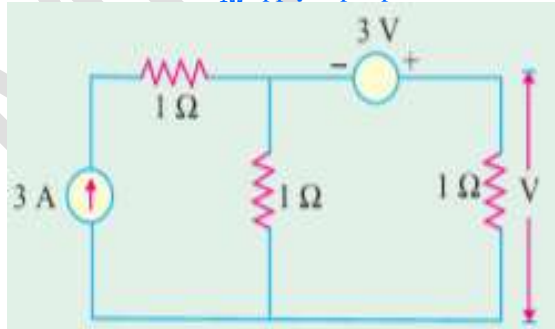**Solution:**

When 3A active,

$$I' = \frac{3}{2} = 1.5\text{A} \quad (\downarrow)$$

When 3V active,


$$I'' = \frac{3}{2} = 1.5\text{A} \quad (\downarrow)$$

$$I = 1.5 + 1.5 = 3A \quad (\downarrow)$$

$$\text{Voltage} = 3 \times 1 = 3V \quad (\text{Ans.})$$

$$\text{Power} = I^2 R = 3^2 \times 1 = 9W \quad (\text{Ans.})$$

6. Find out the value of V? [Ans: 70V]

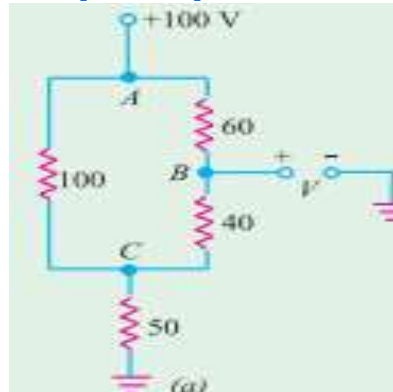


$$\text{Solution: } I_T = \frac{100}{(60+40) \parallel 100+50} = 1A$$

$$I_{40} = \frac{1}{2} = 0.5A$$

(Because of "AC" Parallel resistance are equal. So current division is equal between the two resistance)

$$V = (40 \times 0.5) + 50 = 70V \quad (\text{Ans.})$$

7. Find out the value of R? [Ans: 1Ω]

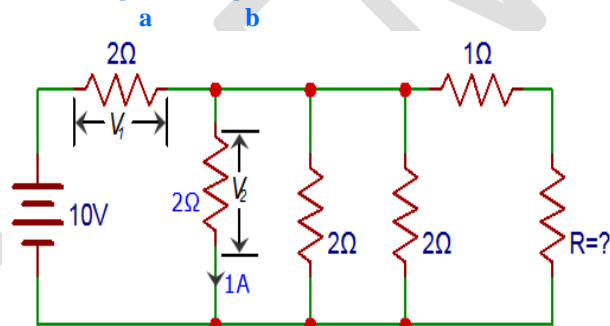

$$\text{Solution: } I_T = \frac{10-2}{2} = 4A$$

Apply KCL point a,

$$I_T = 1 + x$$

$$4 = 1 + x$$

$$x = 3A$$


Apply KCL point b,

$$I_R = 3 - \left(\frac{2}{2} + \frac{2}{2}\right) = 1A$$

$$1 = \frac{2}{1+R}$$

$$R = 1\Omega \quad (\text{Ans.})$$

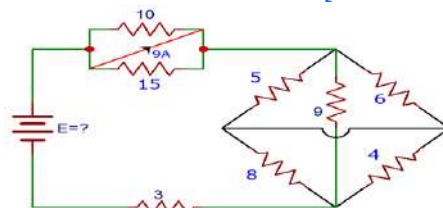8. Find out the value of E? [Ans: 57.35 V]




Solution: Firstly, Simplify this circuit.

$$R_T = (5 \parallel 6 + 8 \parallel 4) \parallel 9 + 3 = 6.3726 \Omega$$

$$V = 6.3726 * 9 = 57.3534 \text{ V} \quad (\text{Ans.})$$

9. Find out the value of R? [Ans: 4 Ω]

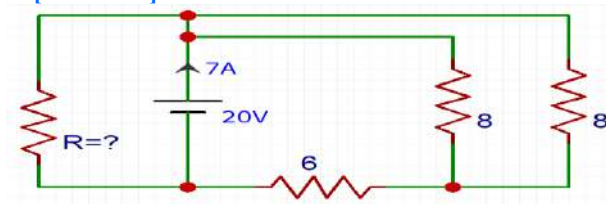

Solution: $R = (8 \parallel 8) + 6 = 10 \Omega$ $I = \frac{20}{10} = 2 \text{ A}$


Apply KCL,

$$I_R = 7 - 2 = 5 \text{ A}$$

$$R = \frac{20}{5} = 4 \Omega \quad (\text{Ans.})$$

10. Find out the value of V?

[Ans: 1.2 V]

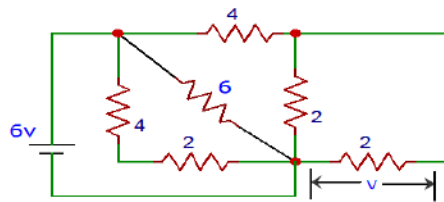

Solution: Simplify this circuit. How it will be simplified. Then solve it own style.

$$R_T = 3 \parallel 5 = 1.875 \Omega, I = \frac{6}{1.875} = 3.2 \text{ A}$$


$$I_4 = 3.2 - 2 = 1.2 \text{ A}$$

$$I_2 = \frac{1.2}{2} = 0.6 \text{ A}$$

$$V_2 = 0.6 * 2 = 1.2 \text{ V} \quad (\text{Ans.})$$

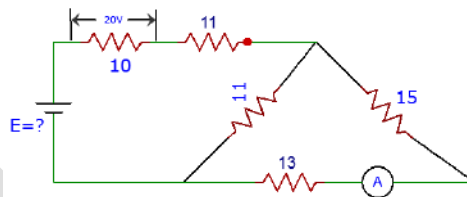11. Find out the value of E and Ammeter Current?

[Ans: V=57.79 Volt, Ammeter current= 0.564 Amp]



Solution: $I_T = \frac{20}{10} = 2 \text{ A}$


Applying current divider rule, $I_A = \frac{2 * 11}{11 + 15 + 13} = 0.564 \text{ A} \quad (\text{Ans.})$

Voltage drop of Ammeter branch = $0.564 * (15 + 13) = 15.795 \text{ V}$

Total voltage $E = 20 + (11 * 2) + 15.795 = 57.795 \text{ V} \quad (\text{Ans.})$

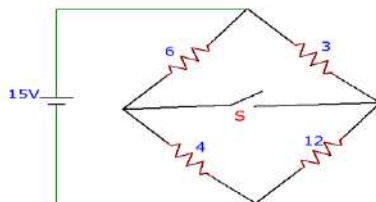12. Find out the value of I_T ? [When S is open and, S is close]

[Ans: I_T (S closed)=3A I_T (S open)=2.5A]




Solution: When S is open,

$$R_T = 10 \parallel 15 = 6 \Omega \quad I_T = \frac{15}{6} = 2.5 \text{ A} \quad (\text{Ans.})$$

When S is closed,

$$R_T = 6 \parallel 3 + 4 \parallel 12 = 5\Omega \quad I_T = \frac{15}{5} = 3A \quad (\text{Ans.})$$

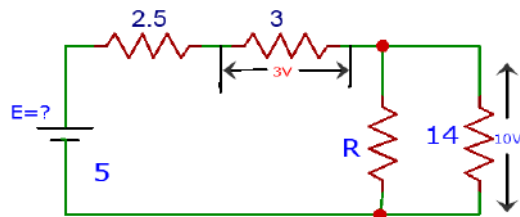13. Find out the value of E, R? [Ans: V=15.5 Volt, R=35Ω] *




Solution: Applying KCL,

$$I_R = I_T - I_{14} = 1 - \frac{10}{14} = 0.2857A$$

$$R = \frac{10}{0.2857} = 35\Omega \quad (\text{Ans.})$$

$$\text{Total voltage } E = 3 + 10 + (2.5 \times 1) = 15.5V \quad (\text{Ans.})$$

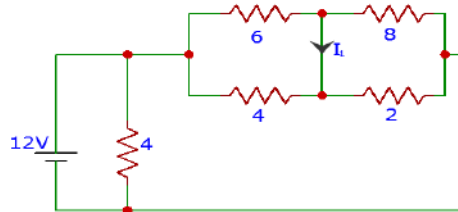14. Find out the value of I_T , I_1 ? [Ans: $I_T=6$ Amp, $I_1=0.6$ Amp]



$$\text{Solution: } I_T = \frac{V}{R_T} = \frac{12}{(8 \parallel 2 + 6 \parallel 4) \parallel 4} = 6A \quad (\text{Ans.})$$


Apply KCL,

$$I_6 = I_1 + I_8$$

$$\frac{3 \times 4}{6 + 4} = I_1 + \frac{3 \times 2}{8 + 2}$$

$$I_1 = 0.6A \quad (\text{Ans.})$$

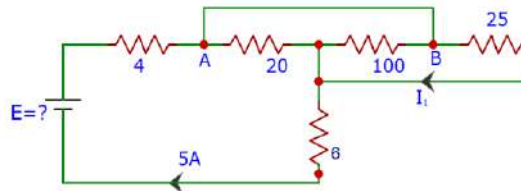15. Find out the value of E, I_1 ? [Ans: E=100 Volt, $I_1=2$ Amp]



Solution: Very easy circuit. Don't fear. Apply point method. So, let's try.

$$R_T = (20 \parallel 100 \parallel 25) + 10 = 20\Omega$$

$$E = 5 \times 20 = 100V \quad (\text{Ans.})$$

$$V_{25} = 100 - (10 \times 5) = 50V$$

$$I_1 = \frac{50}{25} = 2A \quad (\text{Ans.})$$

Special Thanks to
Meson Chakma
EEE, DUET.